

ELEC 5280 Homework 2

Due on March 24th, 2024 (Sun.). You must submit your homework online via Canvas.

Problem 1

The purpose of this exercise is to help you to understand the impact of parasitic resistance on the RF characteristics performance of a MOSFET. Using the **TSMC 22nm CMOS PDK (Cadence library name: tsmcN22)** provided (*see [Tutorial]02 Homework 2 TSMC 22nm CMOS Characterization with Cadence), simulate the NMOS model named “**nmos_rf_lvt_nw**” with $W = 1\ \mu\text{m}$, $L = 30\ \text{nm}$ and number of fingers = 4, i.e., the total width = $4\ \mu\text{m}$, in Cadence. For 22nm process, you can use ideal inductors and capacitors to bias the device to set $V_{gs} = 0.4\ \text{V}$ and $V_{ds} = 0.5\ \text{V}$. Perform a S-parameter simulation from **200 MHz to 200 GHz**.

Table 1. Equivalent circuit model components based on Y-parameters.

Circuit Model Component	Expression
Input Resistance	$R_{in} = R_e \left(\frac{1}{Y_{11}} \right)$
Output Resistance	$R_{out} = \frac{1}{R_e(Y_{22})}$
Input Capacitance	$C_{in} = \frac{\partial}{\partial \omega} \left[\frac{1}{\text{Im} \left(\frac{-1}{Y_{11}} \right)} \right]$
Output Capacitance	$C_{out} = \frac{\partial}{\partial \omega} [\text{Im}(Y_{22})]$
Transconductance	$g_m = \text{Re}(Y_{21})$
Feedback Capacitance	$C_{fb} = \frac{\partial}{\partial \omega} [\text{Im}(-Y_{12})]$

 


Figure 1. Test bench for an NMOS device.

- Figure 2 presents the schematic of a single-ended common-source LNA. Your task is to modify this schematic into a differential topology. For tasks (e) to (i), you should make modifications without adding the capacitor C_d and the inductor L_x . For tasks (j) and (k), incorporate C_d into your design. Finally, for task (l), include L_x in the schematic.

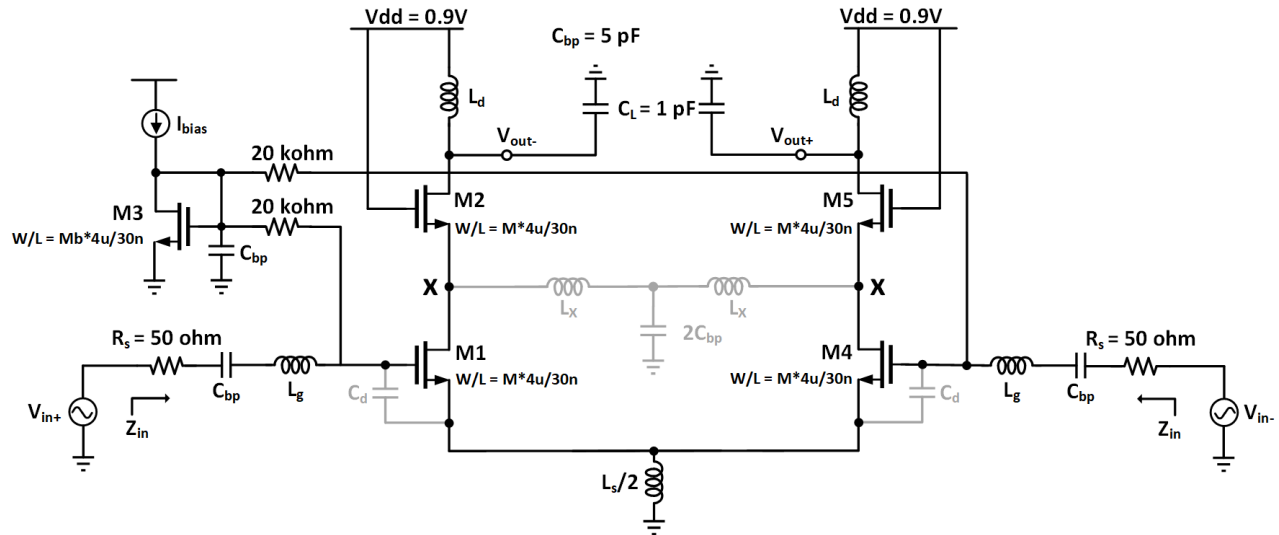


Figure 3. Schematic of the corresponding differential LNA.

- Simulate the single transistor M1. Plot g_m vs. I_{den1} (current density) and f_T vs. I_{den1} by sweeping I_{ds} , M1 with a fixed width, e.g., $4\mu m$. (Hint: For 22nm transistors, minimum finger number is 4. To simplify calculations, we will standardize the finger width at $1\mu m$. Therefore, the total width = $M \times \text{finger width} \times \text{finger number} = M \times 4\mu m$)
- Determine I_{bias} and M (Multiplier of M1 and M2) that gives the optimal f_T and g_m for minimizing NF. What is resulting input resonant circuit Q ? (For the size of transistor M3, M_b is typically very smaller than M , e.g., $M_b = 10\%M$)
- Determine L_g and L_s using C_{gs} and f_T to provide the required input matching. Assume L_s and L_g have a Q of 15 at f_0 , compute the series resistance value and include it in the simulation (use 'ind' and 'res' from 'analogLib').
- Determine L_d such that the output node is tuned at f_0 . Assume L_d have a Q of 15 at f_0 , compute the series resistance value and include it in the simulation (use 'ind' and 'res' from 'analogLib').
- Plot the gain (V_{out}/V_{in}), noise figure (NF) and input impedance (Z_{in}) vs. frequency from 0.1 to 50 GHz.
- Perform a PSS analysis at f_0 to determine the 1-dB compression of this LNA by sweeping the input port power.
- Using PSS analysis, perform a two-tone test to determine the IIP3 of the LNA using signals at f_0 and $f_0 + 800\text{MHz}$. (Optional: You can use hb and PAC analysis to simulate the IIP3 again and compare results for **bonus credits**).
- Using sp analysis, plot the K factor vs. frequency from 0.1 to 50 GHz. Comment on the stability of your designed LNA based on the simulation result.
- Using sp analysis, plot noise circles with noise ranges from 1 dB to 10 dB and gain circles with gain ranges from 10 dB to 20 dB, both at f_0 . **Comment on the trade-off between gain and noise based on the circles.**
- Now, add C_d between the gate and source terminal of M1, plot NF at f_0 vs. C_d , make sure that you adjust L_g and L_s for each value of C_d to maintain the input matching at f_0 . How much is the improvement in NF? What happened to the amplifier gain?
- With the C_d and the L_g , perform a sweep of the input device width, is there a new optimal width that gives lower NF? If so, what is it and what is the NF?
- Now, add L_x at the cascode node by first estimating the parasitic capacitance at node X. How much is the improvement in NF? What happened to the amplifier gain?

Hint:

In our design of a Low Noise Amplifier (LNA) using 22nm technology, we utilized two noise reduction techniques. The first is based on P. Andreani's method from the *IEEE TCAS-II* in 2001, which uses a capacitive load (C_d) to reduce the coupling between the Q factor of the input resonant circuit and the gate-source capacitance (C_{gs}). The second technique, proposed by H. Samavati in the *IEEE JSSC* in 2000, focuses on impedance enhancement.

While our design does not incorporate the latest advancements, such as the 65nm common-gate LNA by X. Wu presented at the *IEEE IWS* in 2019, or the 22nm FD-SOI two-stage LNA by Z. Zong from the *IEEE RFIC* Symposium in 2021, these cutting-edge designs represent potential future directions for enhancing our LNA design.

Reference Papers

- [1] Thomas H. Lee, *The Design of CMOS Radio-Frequency Integrated Circuits*, 2nd Edition, 2004.
- [2] X. Wu, M. Kalantari, D. H. Shin and C. Patrick Yue, "A 24-32GHz gm-boosted LNA with Triple Coupling Input Transformer for 5G Applications," 2019 IEEE MTT-S International Wireless Symposium (IWS), Guangzhou, China, 2019.
- [3] Z. Zong et al., "A 39GHz T/R front-end module achieving 25.6% PAEmax, 20dBm Psat, 5.7dB NF, and -13dBm IIP3 in 22nm FD-SOI for 5G communications," 2021 IEEE Radio Frequency Integrated Circuits Symposium (RFIC), Atlanta, GA, USA, 2021.
- [4] P. Andreani and H. Sjöland, "Noise Optimization of an Inductively Degenerated CMOS Low Noise Amplifier," *IEEE TRANSACTIONS ON CIRCUITS AND SYSTEMS—II: ANALOG AND DIGITAL SIGNAL PROCESSING*, VOL. 48, NO. 9, SEPTEMBER 2001 835.
- [6] H. Samavati, H. R. Rategh, T. H. Lee, "A 5-GHz CMOS Wireless LAN Receiver Front End," *IEEE JOURNAL OF SOLID-STATE CIRCUITS*, VOL. 35, NO. 5, MAY 2000, pp.765.